

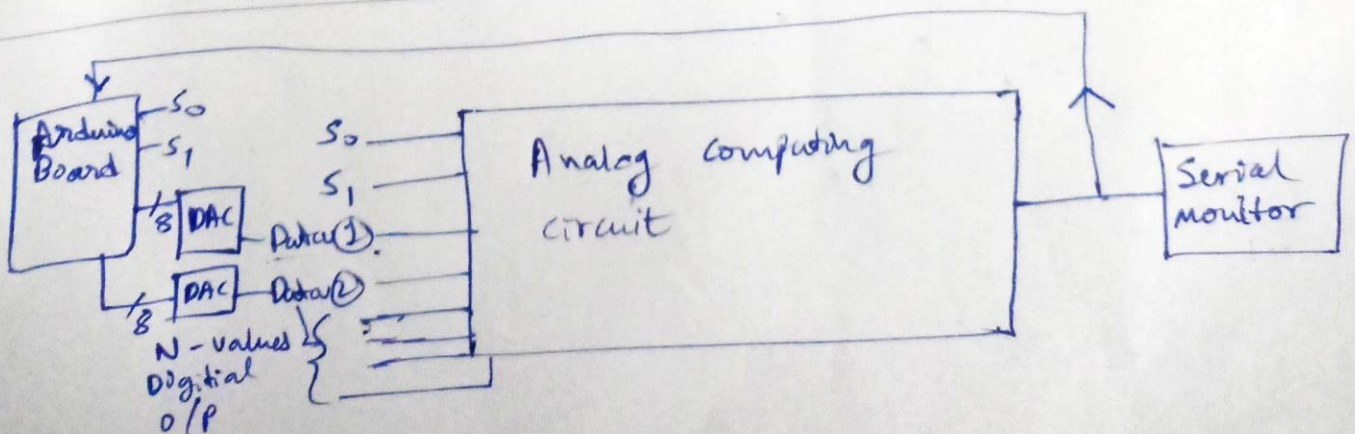


Final Core Analog computing circuit

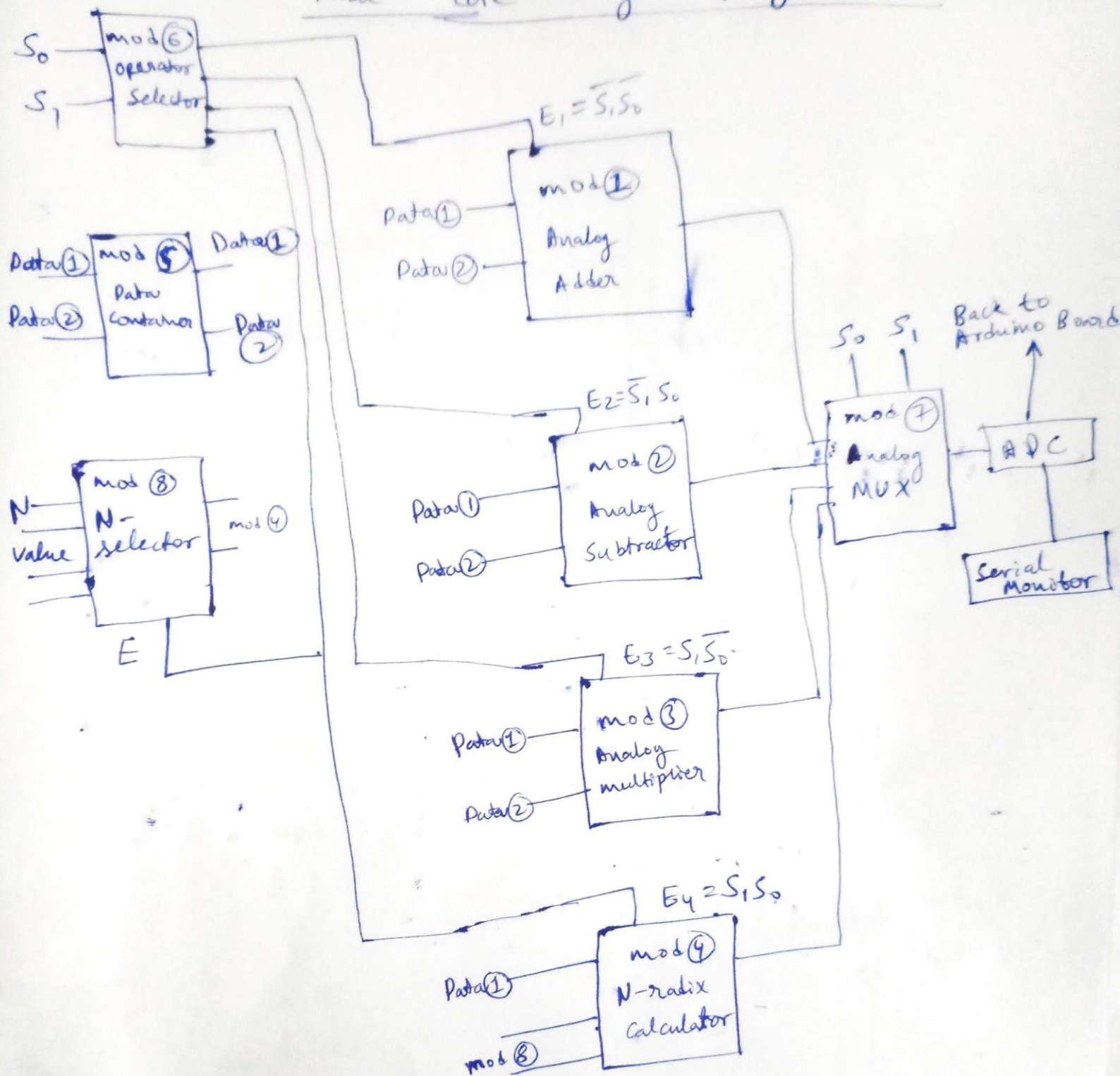


Module ① { Analog Adder }

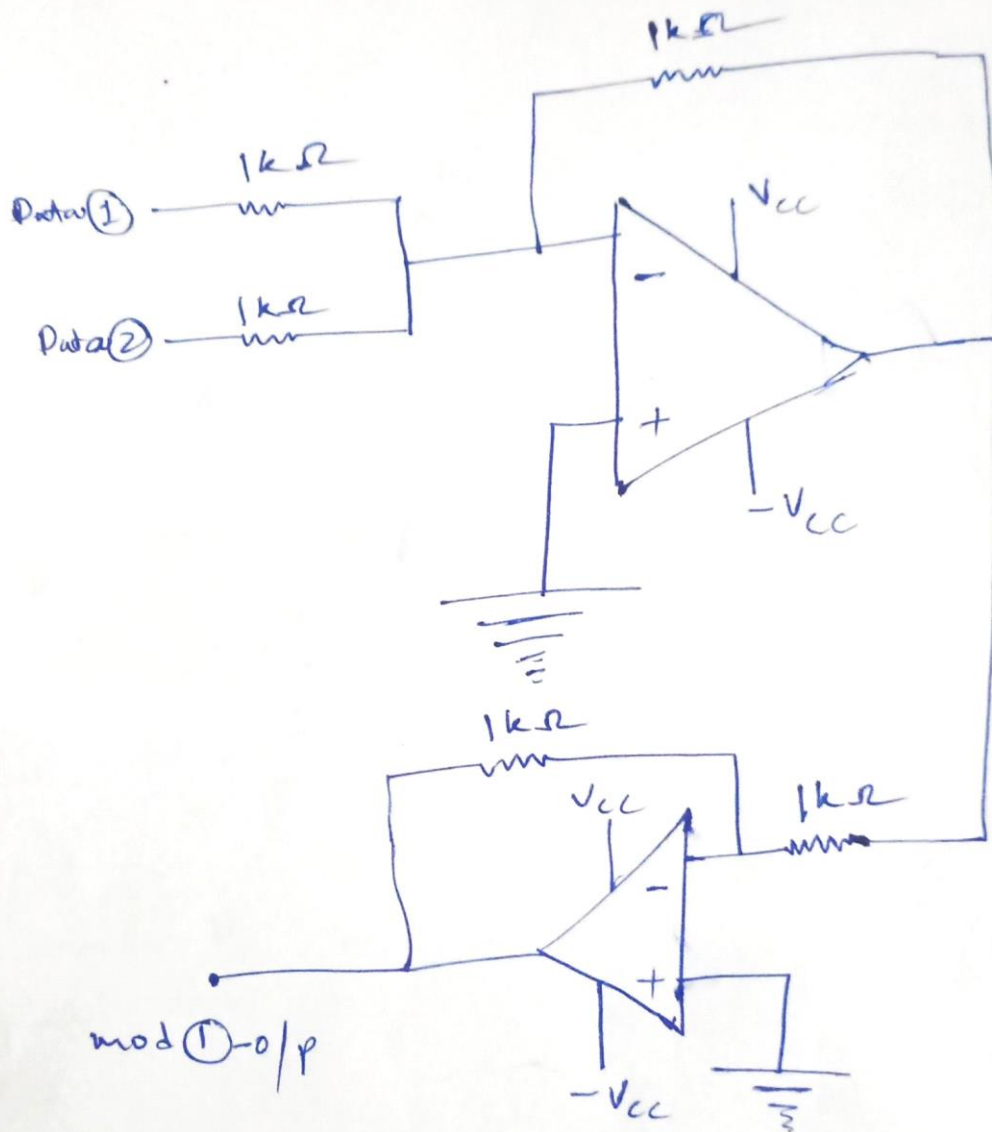


→ V_{cc} and $-V_{cc}$ are controlled by the help of module ⑥.



Module (2) { Analog Subtractor }

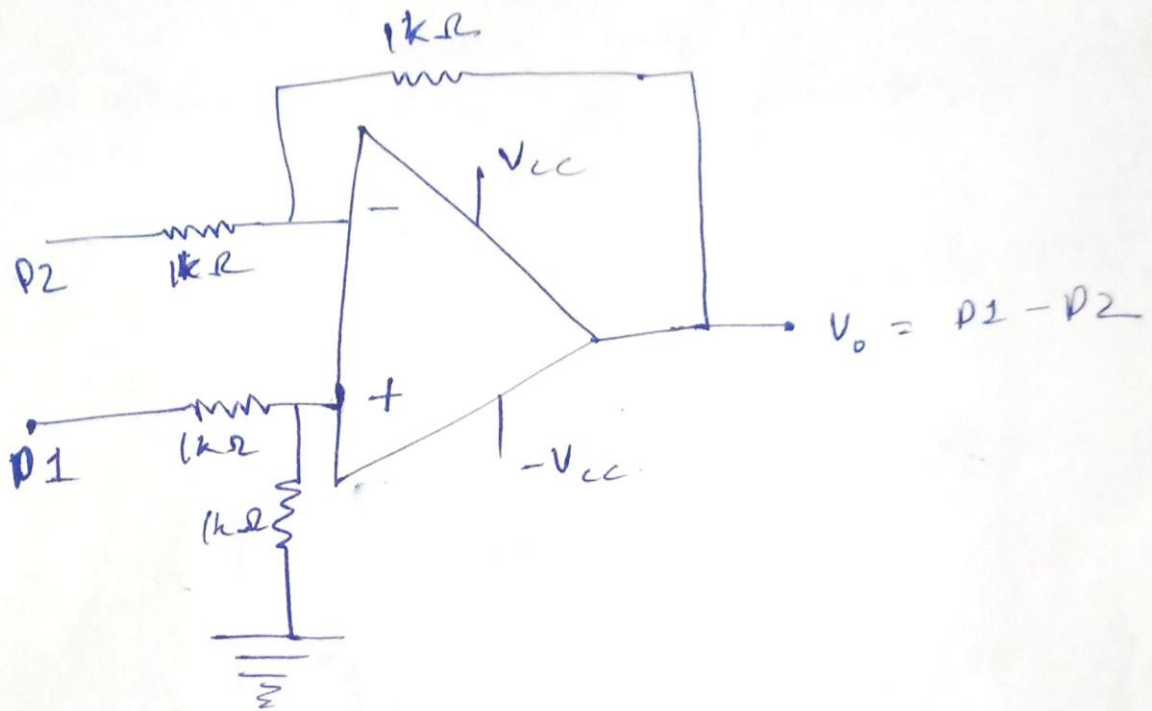

→ V_{cc} and $-V_{cc}$ are controlled with the help of module (6).


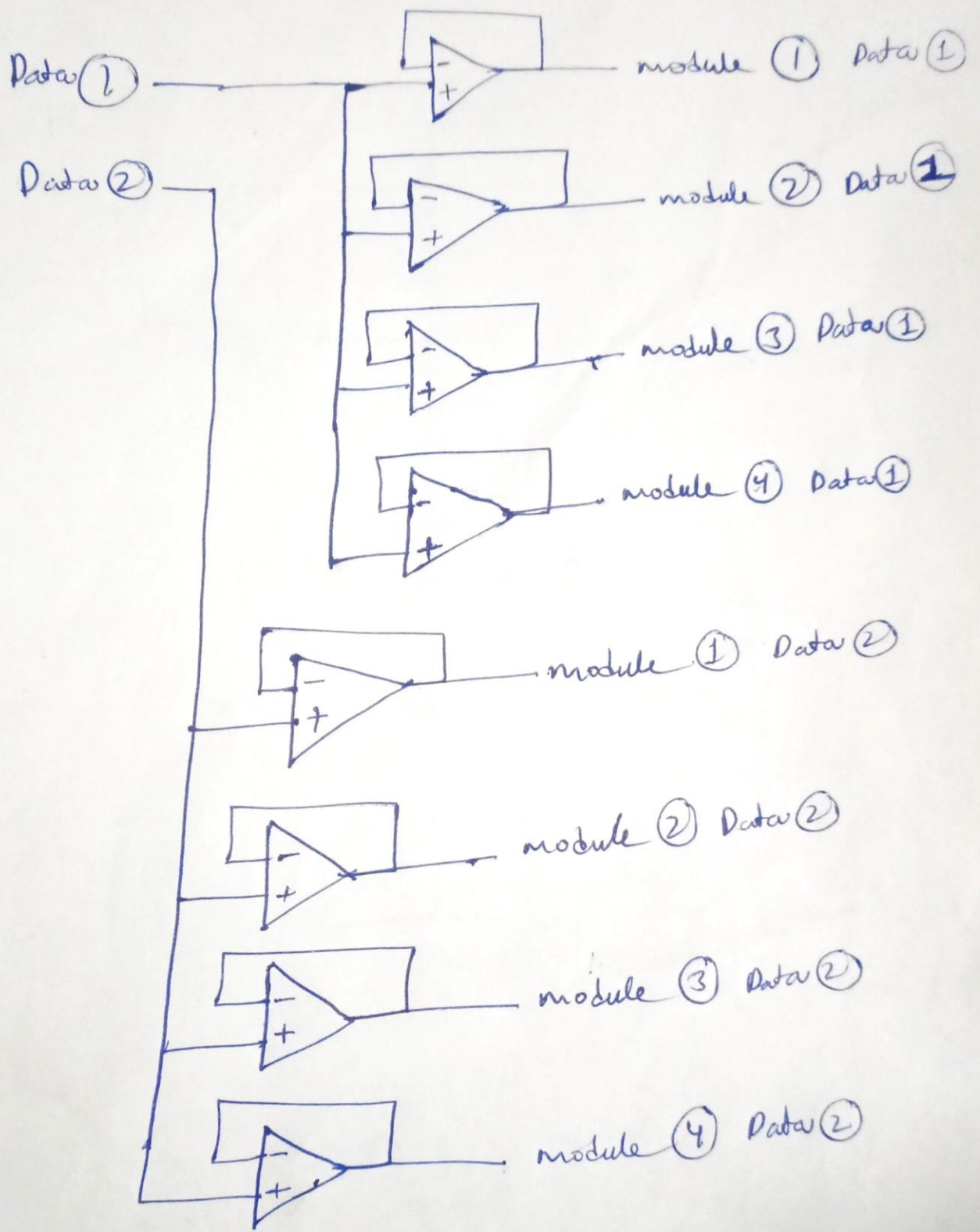


module 5
 { Data container }

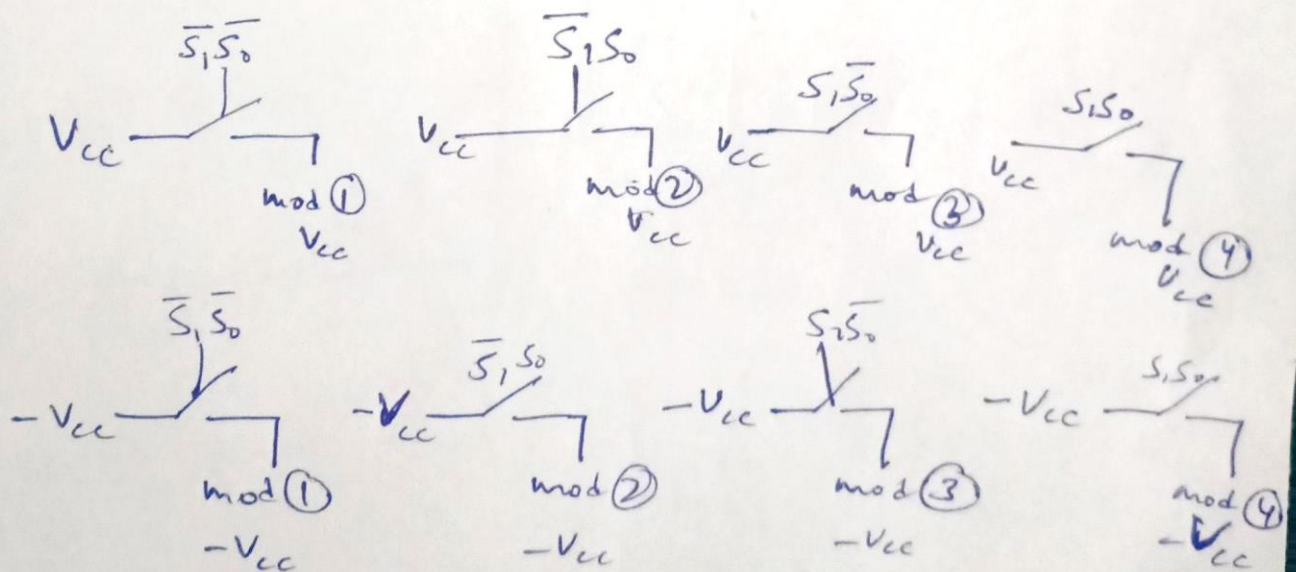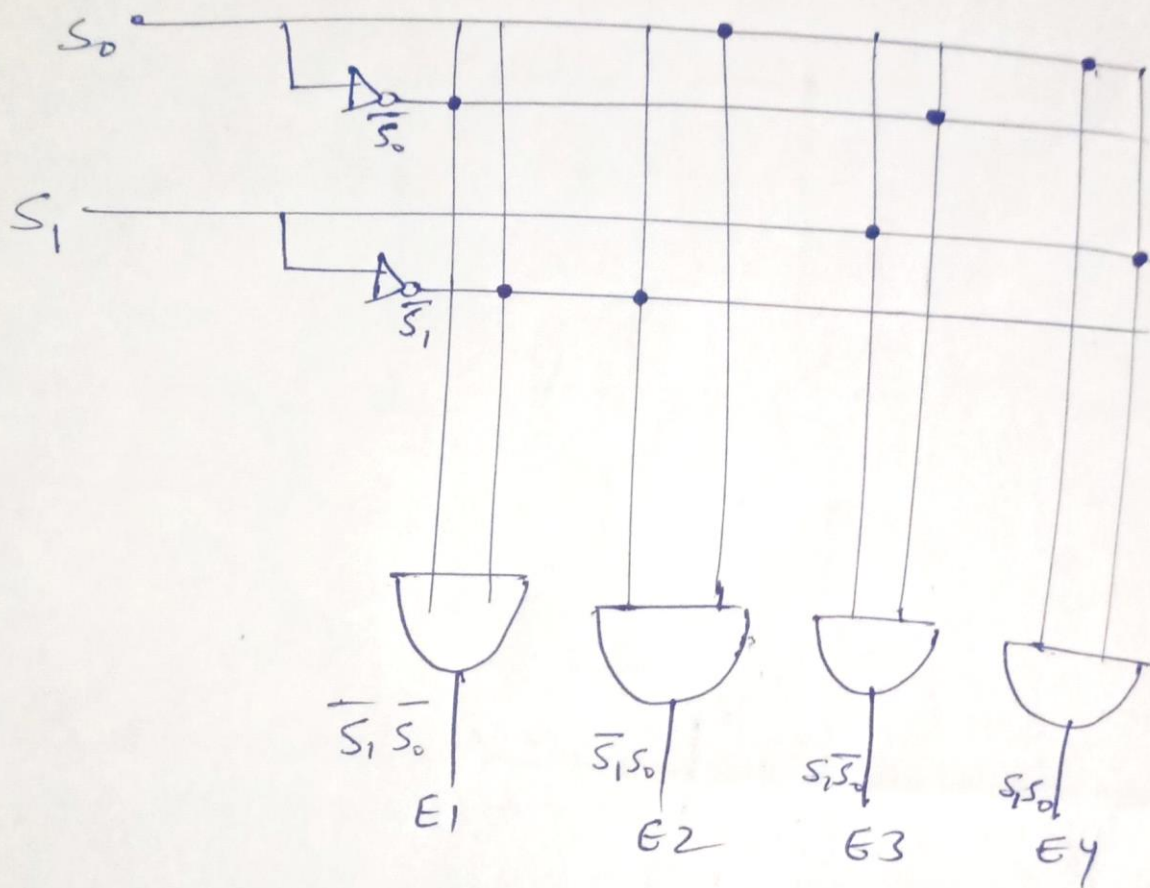

- * Switches are implemented using CD 4066.
- * Not gates are implemented using 74HC04.
- * And gates are implemented using 74HC08.

module (7)

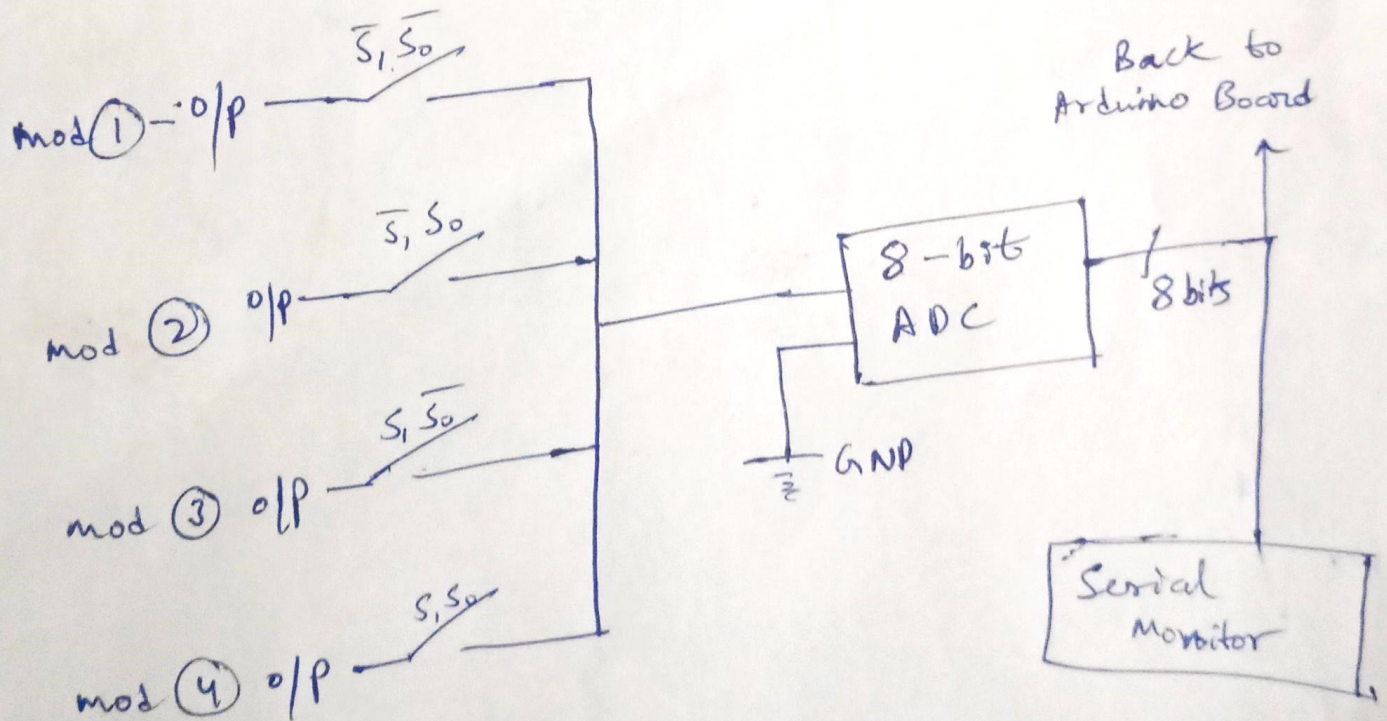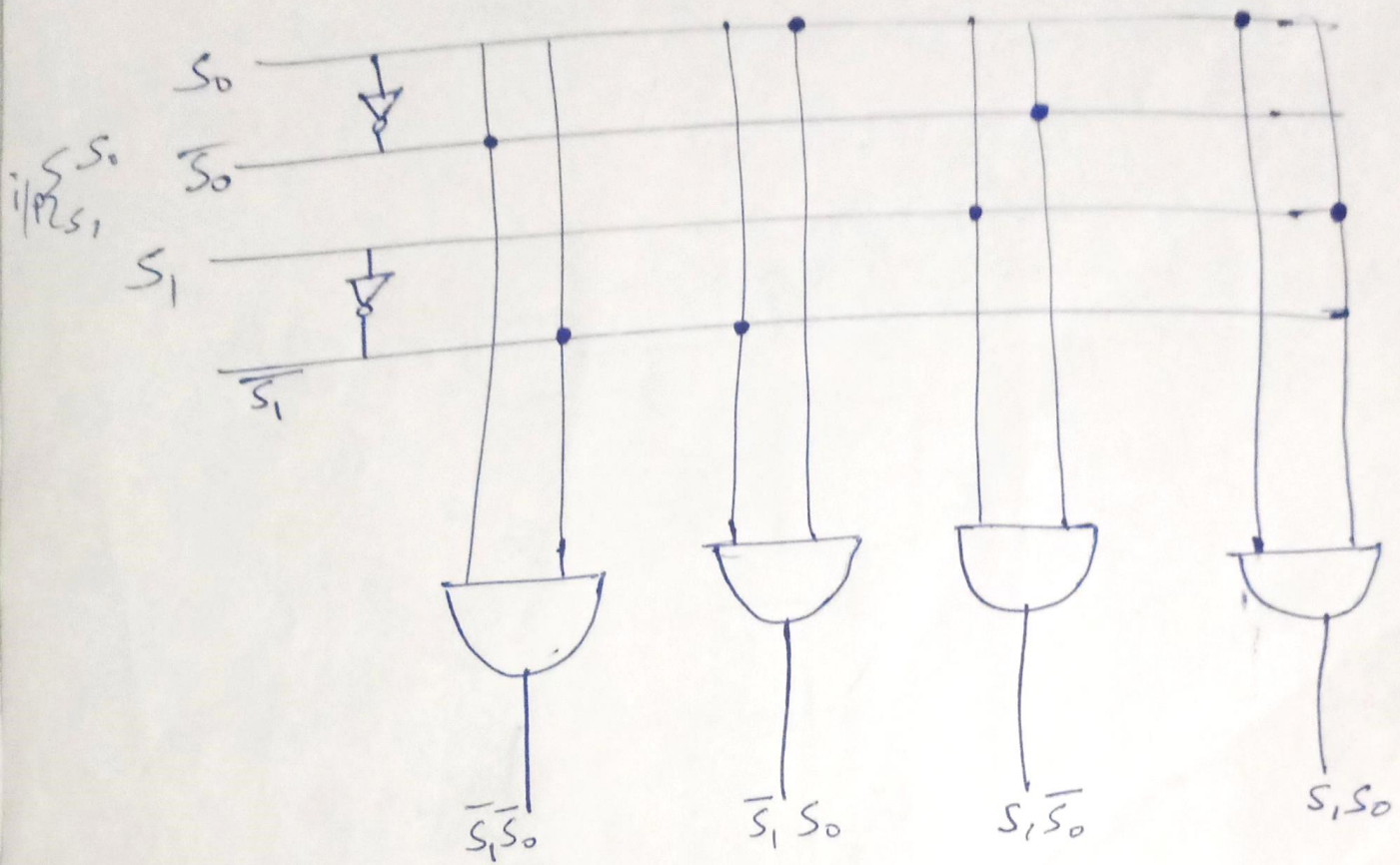

module ⑧ { N-selector }

N-Value { 4-bits Digital } — $I_3 I_2 I_1 I_0$

